

Outstanding Material from Lecture 1

EL GY 6463: Advanced Hardware Design


Instructor: Siddharth Garg

Finite State Machines: Introduction

- **Combinational logic**: output depends on the current input only
- **Finite State Machine**: output depends on input *and* current state

 Example: what is my current speed?

- Given only speedometer reading $s(t)$: output = $s(t)$
- Given only accelerometer reading $a(t)$:



**But is this a finite state machine?
Why or why not?**

FSM: Formal Model


- A finite set of *states*: S
 - An initial state: $s_0 \in S$
- A finite set of *inputs*: Σ
- A finite set of *outputs*: Γ
- A state transition function $\delta : S \times \Sigma \rightarrow S$
- An output function ω
 - **Moore machine** $\omega : S \rightarrow \Gamma$ ← Output depends only on current state
 - **Mealy machine** $\omega : S \times \Sigma \rightarrow \Gamma$ ← Output depends on current state and input

FSM Example: Edge Detector

- **Goal:** detect 0->1 and 1->0 transitions in a sequence of inputs. Output a 1 when a transition occurs, zero otherwise.

Input: 00**1**0**1**111**1**000**0**1000

Output: 00111000010001100

 

- *states* $S = \{START, AT_1, AT_0, EDGE_10, EDGE_01\}$


- Initial state: $s_0 = START$

- *Inputs* $\Sigma = \{0,1\}$


- *Outputs* $\Gamma = \{0,1\}$

Is this a Mealy or a Moore machine?

Clocked Implementation of a Moore FSM

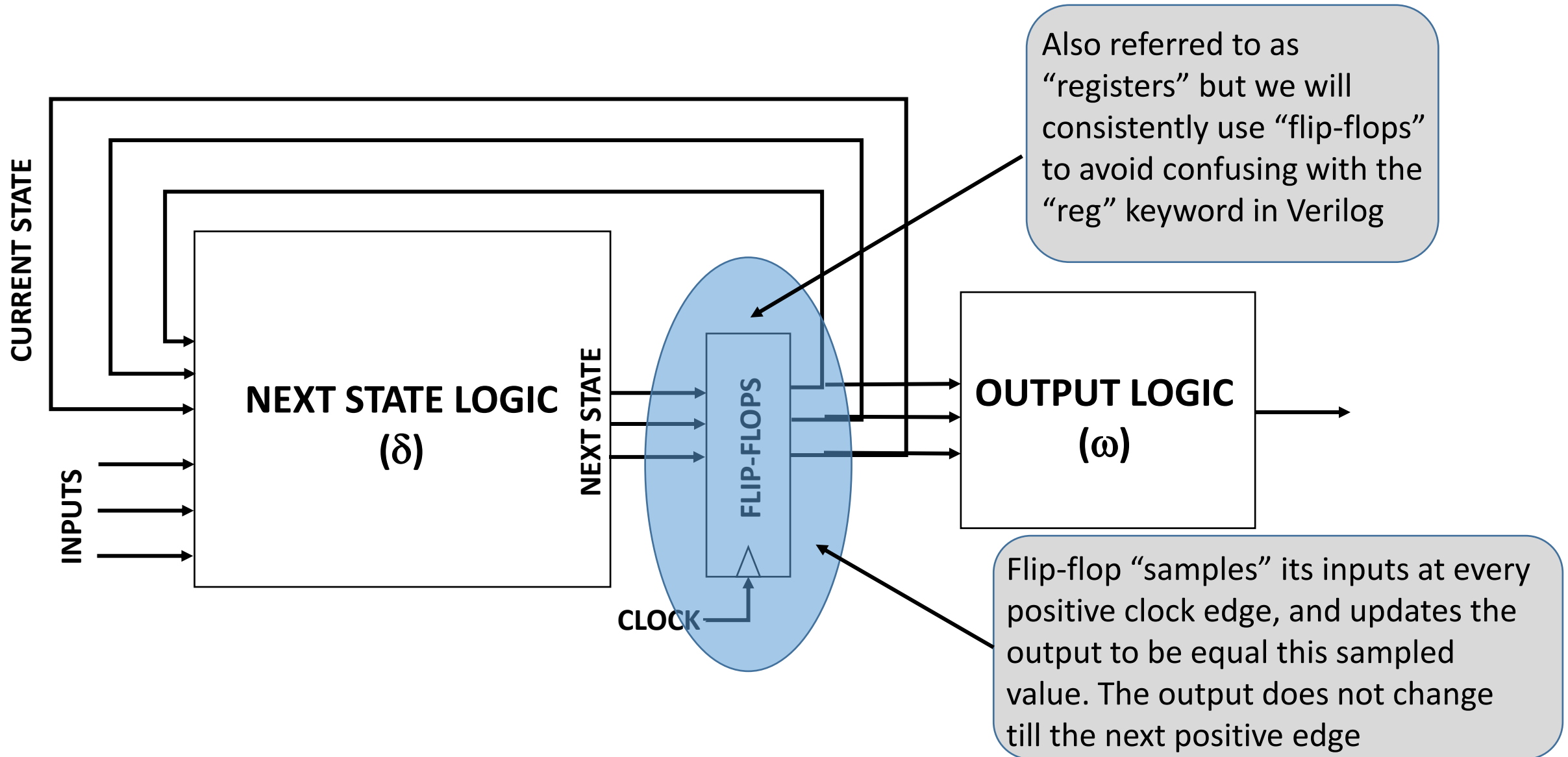

Flip-flops in Verilog

 

If reset = 1, output Q = 0.

- Asynchronous: Q = 0 as soon as reset becomes 1
- Synchronous: Q = 0 at next positive edge

D Flip-flop with Asynchronous Reset.

```
module dff ( input D, input reset,  
             input clock, output reg Q );
```

```
    always @ (posedge clock, posedge reset) begin  
        if (reset)  
            Q <= 0;  
        else  
            Q <= D;  
        end  
    endmodule
```

when clock transitions from 0 to 1


or reset transitions from 0 to 1

- **Non-blocking assignment**
(remember that = is a blocking assignment)
- Rule of thumb: use non-blocking when always block is edge triggered. More on this later.

What about synchronous reset?

Edge Detector FSM in Verilog

 - Let's implement the **sequential portion** first
 - At positive clock edge, current state <= next state



```
module edge_detect ( input in, input clock, input reset, output reg out);
```

```
    reg [2:0] current_state, next_state;
```

Three bits. Why?

```
    localparam START = 0, AT_1 = 1, AT_0 = 2, EDGE_10 = 3, EDGE_01 = 4;
```

```
    //localparam START = 3'b000, AT_1 = 3'b001, AT_2 = 3'b010 ... ;
```

```
    always @ (posedge clock, posedge reset) begin
```

```
        if (reset)
```

```
            current_state <= START;
```

```
        else
```

```
            current_state <= next_state;
```

```
    end
```

```
endmodule
```

Three bits.

Constant defined only
within the scope of
current module

Edge Detector FSM in Verilog (In-Class Exercise)

- Now let's implement the **next state and output logic**

```
module edge_detect (input in, input clock, input reset, output reg out);  
  // sequential code from previous slide
```

```
  always @ (current_state, in) begin //always @ (*)
```

```
    out = 0;
```

```
    next_state = current_state;
```

```
    case (current_state)
```

```
      START: if (in) next_state = AT_1;
```

```
             else next_state = AT_0;
```

```
      AT_1:  if (~in) next_state = EDGE_10;
```

```
      AT_0:  if (in) next_state = EDGE_01;
```

```
      EDGE_10: begin
```

```
        out = 1;
```

```
        if (in) next_state = EDGE_01;
```

```
        else next_state = AT_0;
```

```
      end
```

```
      EDGE_01: //DO THIS
```


```
      default: begin out = 1'bX; next_state = 3'bX; end
```

X: don't care

```
    endcase
```

```
  end
```

```
endmodule
```

 


Similar to C
case
statement

Current_state = 5,6,7

Solution

```
EDGE_01: begin
    out = 1;
    if (~in) next_state = EDGE_10;
    else next_state = AT_1;
end
```

Simulation Output

 


VSIM 61> run

```
#          0 in=0, clock=0, reset=0, out=x
#          20 in=0, clock=1, reset=0, out=x
#          40 in=0, clock=0, reset=0, out=x
#          50 in=0, clock=0, reset=1, out=0
#          60 in=0, clock=1, reset=1, out=0
#          80 in=0, clock=0, reset=1, out=0
#         100 in=0, clock=1, reset=1, out=0
#         120 in=0, clock=0, reset=0, out=0
#         140 in=0, clock=1, reset=0, out=0
#         160 in=0, clock=0, reset=0, out=0
#         180 in=0, clock=1, reset=0, out=0
#         200 in=1, clock=0, reset=0, out=0
#         220 in=1, clock=1, reset=0, out=1
#         240 in=1, clock=0, reset=0, out=1
#         260 in=1, clock=1, reset=0, out=0
#         280 in=1, clock=0, reset=0, out=0
```

Mealy Machine

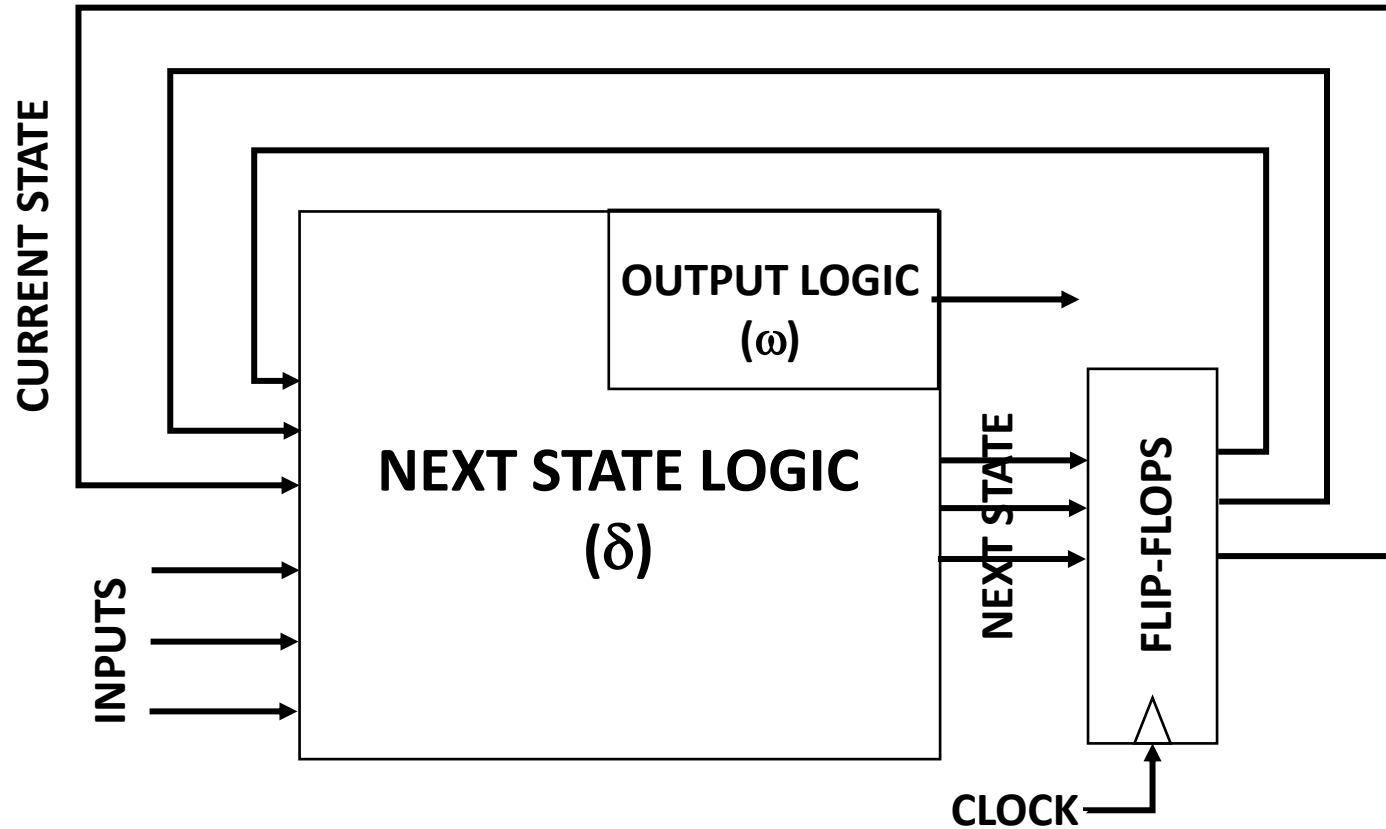
- Mealy machine: output depends on state *and* input



Direct path between inputs and outputs that does not pass through a flip-flop

- Pros:
 - Fewer states
 - Output more “responsive” to input
- Cons:
 - Unstable outputs
 - Cascading Mealy machines?

Mealy Machine: Verilog Implementation

 

```
module edge_detect ( input in, input clock,
                    input reset, output reg
                    out);


reg [1:0] current_state, next_state;

localparam START = 0, AT_1 = 1, AT_0 = 2;

always @ (posedge clock, posedge reset) begin
    if (reset)
        current_state <= START;
    else
        current_state <= next_state;
end
.....
endmodule
```

Mealy Machine: Verilog Implementation (In Class Exercise)


```
module edge_detect (input in, input clock, input reset, output reg out);  
  // sequential code from previous slide  
  always @ (current_state, in) begin //always @ (*)  
    out = 0;  
    next_state = current_state;  
    case (current_state)  
      START: if (in) next_state = AT_1;  
             else next_state = AT_0;  
      AT_1:  begin  
                if (~in) begin  
                  out = 1;  
                  next_state = AT_0;  
                end  
            end  
      AT_0:  //DO THIS  
      default:  
    endcase  
  end  
endmodule
```

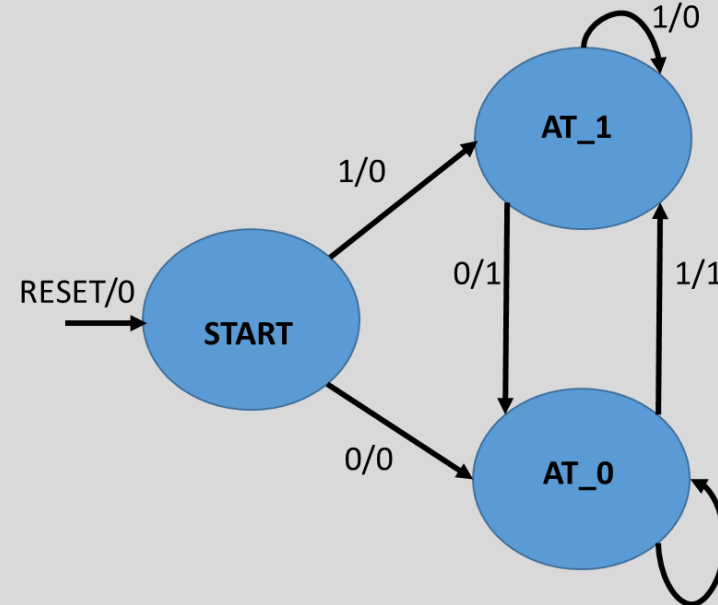

Solution

```
AT_0:  begin
        if (in) begin
            out = 1;
            next_state = AT_1;
        end
    end
```


Simulation Output

 

VSIM 68> run

```
#          0 in=0, clock=0, reset=0, out=x
#          20 in=0, clock=1, reset=0, out=x
#          40 in=0, clock=0, reset=0, out=x
#          50 in=0, clock=0, reset=1, out=0
#          60 in=0, clock=1, reset=1, out=0
#          80 in=0, clock=0, reset=1, out=0
#         100 in=0, clock=1, reset=1, out=0
#         120 in=0, clock=0, reset=0, out=0
#         140 in=0, clock=1, reset=0, out=0
#         160 in=0, clock=0, reset=0, out=0
#         180 in=0, clock=1, reset=0, out=0
#         200 in=1, clock=0, reset=0, out=1
#         220 in=1, clock=1, reset=0, out=0
#         240 in=1, clock=0, reset=0, out=0
#         260 in=1, clock=1, reset=0, out=0
#         280 in=1, clock=0, reset=0, out=0
```

Blocking Vs. Non-blocking Assignments

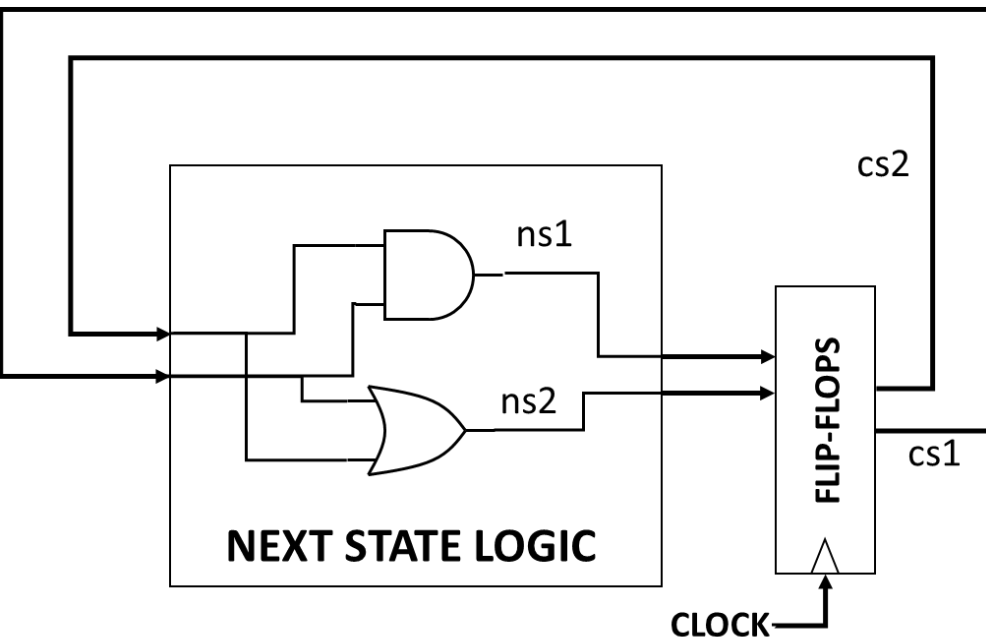


```
// combinational part
always @(cs1, cs2) begin
    ns1 = cs & cs2;
    ns2 = cs1 | cs2;
end
//sequential part
always @ (posedge clock) begin
    cs1 <= ns1;
    cs2 <= ns2;
end
```

OR

```
// sequential + combinational part
always @(posedge clcok) begin
    cs1 <= cs & cs2;
    cs2 <= cs1 | cs2;
end
```

Both LHSs evaluated first;
then assigned to RHSs. As
if the two ops happened in
parallel

Blocking Vs. Non-blocking Assignments

 

```
// combinational and sequential part
```

```
always @(posedge clock) begin
```

```
    cs1 = cs & cs2;
```

```
    cs2 = cs1 | cs2;
```

DOES NOT WORK

```
end
```

```
// Blocking assignments operate in sequence.
```

```
// So first cs1 will become 0 (1&0).
```

```
// Now both cs1 and cs2 are 0.
```

```
// The next statement executes, and cs2 remains zero.
```

OR

```
// sequential + combinational part
```

```
always @(posedge clk) begin
```

```
    cs1 <= cs & cs2;
```

```
    cs2 <= cs1 | cs2;
```

```
end
```

Will operate correctly regardless of order in which these statements are written!!

Lecture 2: Modeling Complex Designs

EL GY 6463: Advanced Hardware Design

Instructor: Siddharth Garg

Procedural Modeling of Combinational Functions

- Expressing control flow

- Ternary operator
- If-else construct
- Case construct

```
module mux( input a,
            input b,
            input sel,
            output c);

  assign c = (sel)? a : b;

endmodule
```

condition If true If false

```
module mux( input a,
            input b,
            input sel,
            output reg c);

  always @ (*) begin

    if (sel==1)
      c = 1;
    else
      c = 0;

  end
endmodule
```

Logical equality
(more later)

```
module mux( input a,
            input b,
            input sel,
            output reg c);

  always @ (*) begin
    case (sel)
      1'b0: c = a;
      1'b1: c = b;
    endcase
  end
endmodule
```

All cases must
be specified
(use default
case)

For Loops

- Similar to for loops in C/C++. Can only be used inside timed blocks (always, initial)

Array of 8 bits. MSB = 7, LSB = 0

```
module xor8( input [7:0] a,  
             input [7:0] b,  
             output reg [7:0] out);
```

```
reg [7:0] i; ← Loop counter
```

```
always @(*) begin
```

```
    for (i=0; i<8; i=i+1) begin  
        out[i] = a[i] ^ b[i];
```

```
    end
```

```
end
```

```
endmodule
```

```
module xor8( input [7:0] a,  
             input [7:0] b,  
             output [7:0] out);
```

```
assign out = a ^ b;
```

```
endmodule
```

Bit-wise xor

For Loops: a more complex example

- Correlator: $out = \sum_{i=1}^N a[i]b[i] + (1 - a[i])(1 - b[i])$
 - Counts number of occurrences where $a[i] == b[i]$

```
module corr8( input [7:0] a, input [7:0] b, output reg [3:0] out);
```

```
reg [7:0] i;
```

```
always @(*) begin
```

```
    out = 0;
```

```
    for (i=0; i<8; i=i+1) begin
```

```
        out = out + (a[i] ^ b[i]);
```

```
    end
```

```
end
```

```
endmodule
```

Out can be at most 8.

Arithmetic addition

Xnor operator

A Note on Verilog Operators

Don't synthesize. Avoid
unless using in test bench
or for simulation only.

- Arithmetic operators
 - Add (+), subtract (-), multiply (*), divide (/), modulus (%)
 - reg and wire datatypes are interpreted as **unsigned** numbers

Examples:

```
module add(  
    input [3:0] a,  
    input [3:0] b,  
    output [4:0] out);
```

```
    assign out = a + b;  
    //a=4'b0101, b=4'b0001  
    // => c=00110 (5+1=6)  
    //a=4'b1000, b=4'b1000  
    // => c=10000 (8+8=16)  
endmodule
```

Carry out bit

```
module sub(  
    input [3:0] a,  
    input [3:0] b,  
    output [4:0] out);
```

```
    assign out = a - b;  
    //a=4'b0101, b=4'b0001  
    // => c=00100 (5-1=4)  
    //a=4'b0001, b=4'b0010  
    // => c=11111 (1-2=?)  
endmodule
```

What's happening here?

```
module mult(  
    input [3:0] a,  
    input [3:0] b,  
    output [7:0] out);
```

```
    assign out = a * b;  
    //a=4'b1111, b=4'b1111  
    // => c=11100001  
    // (15*15=225)  
endmodule
```

Verilog Operators (Bit-wise Vs. Logical)

- Example: `&` (bit-wise) Vs. `&&` (logical)

Two n-bit operands results in
an n-bit output

```
module bitwise_and(  
    input [3:0] a,  
    input [3:0] b,  
    output [3:0] out);  
  
    assign out = a & b;  
    //a=4'b0101, b=4'b0001  
    // => out =0001  
    //a=4'b1001, b=4'b1011  
    // => c= 1001  
endmodule
```

| (or)
^ (xor)
~^ (xnor)
~ (negation)

Always results in a **single bit**
output. Output is 1 if both
operands are non-zero.

```
module logical_and(  
    input [3:0] a,  
    input [3:0] b,  
    output out);  
  
    assign out = a && b;  
    //a=4'b0101, b=4'b0001  
    // => out = 1  
    //a=4'b0001, b=4'b0000  
    // => out = 0  
endmodule
```

|| (or)
== (equality)
!= (inequality)
! (logical not)
>=, <=, <, >

Typical Use
If (a || b)
If (a==b)
If (a != b)
If (!a)
If (a > b)

For more details:

- Appendix C of T&M
- http://web.engr.oregonstate.edu/~traylor/ece474/lecture_verilog/beamer/verilog_operators.pdf

Verilog Operators (Reduction and Concatenation)

- Compute the parity of an 8 bit string. (Why is this useful)?

```
module parity(input [7:0] str,
              output reg par,
              output reg [8:0] par_str);

reg [2:0] i;
always @(*) begin
    par = str[0];
    for (i=1; i<8; i=i+1) begin
        par = par ^ str[i];
    end
    par_str = {str, par};
end

endmodule
```

Concatenation

```
module parity(input [7:0] str,
              output par);
```

Computes $(str[0] \wedge str[1] \dots str[7])$

```
    assign par = ^str;
    assign par_str = {str, par};

endmodule
```

| (or)
~| (nor)
& (and)
~& (nand)
~^ (xnor)

Homework: Read up on Verilog shift operator (>>, <<).

In-class Exercise

- Write a combinational logic module that takes a 16-bit value as input and counts the number of times the pattern '0101' occurs in it.
 - Tip: $x[\text{base}+\text{width}]$ gives $x[\text{base}+\text{width}-1:\text{base}]$

How big should count be?



```
module pattern_count (input [15:0] str, output reg [4:0] count);  
  
  reg [4:0] i;  
  
  always @ (*) begin  
    count = 0;  
    for (i=0; i<16; i=i+1) begin  
      if (str[i+:4] == 4'b0101)  
        count = count + 1;  
    end  
  end  
end  
endmodule
```

Parameterized Modules

- Parameters allow you to declare constants that can be *externally modified*
 - Unlike local parameters (localparam) that cannot be modified from outside the module

```
module parity #(parameter W = 8)
    (input [W-1:0] str,
     output reg par,
     output reg [W:0] par_str);

    reg [2:0] i;

    always @(*) begin
        par = str[0];
        for (i=1; i<W; i=i+1) begin
            par = par ^ str[i];
        end
        par_str = {str, par};
    end

endmodule
```

Default value of W = 8

```
parity #(8) p1 (str, par, par_str);


parity #(12) p1 (str, par, par_str);
```

Finite State Machines (Data path and Control path Synthesis)


- Say you want to build a multiplier but only have access to adders and comparators.
 - Solution: repeated addition. Simple Verilog combinational description

```
module mult #(parameter W = 8)
    (input [W-1:0] x, input [W-1:0] y, output reg [2*W-1:0] out);

     reg [W-1:0] i;    Will work in
                     simulation but does
                     not synthesize?
    always @(*) begin
        out = 0;
        for (i=0; i<y; i=i+1) begin
            out = out + x;
        end
    end
endmodule
```



 Better Solution: Use One Adder Repeatedly




```
module myreg
# (parameter W=8)
(input [W-1:0] xin,
 input xload,
 input xclear,
 input clk,
 output reg [W-1:0] xout);

always @ (posedge clk) begin
    if(xclear)
        xout = 0;
    else if (xload)
        xout = xin;
end

endmodule
```

 Better Solution: Use One Adder Repeatedly




```
module adder
# (parameter W = 8)
(input [W-1:0] in1,
 input [2*W-1:0] in2,
 output reg [2*W-1:0] out);

//the first operand is 0-extended
always @ (*) begin
    out = in1 + in2;
end

endmodule
```

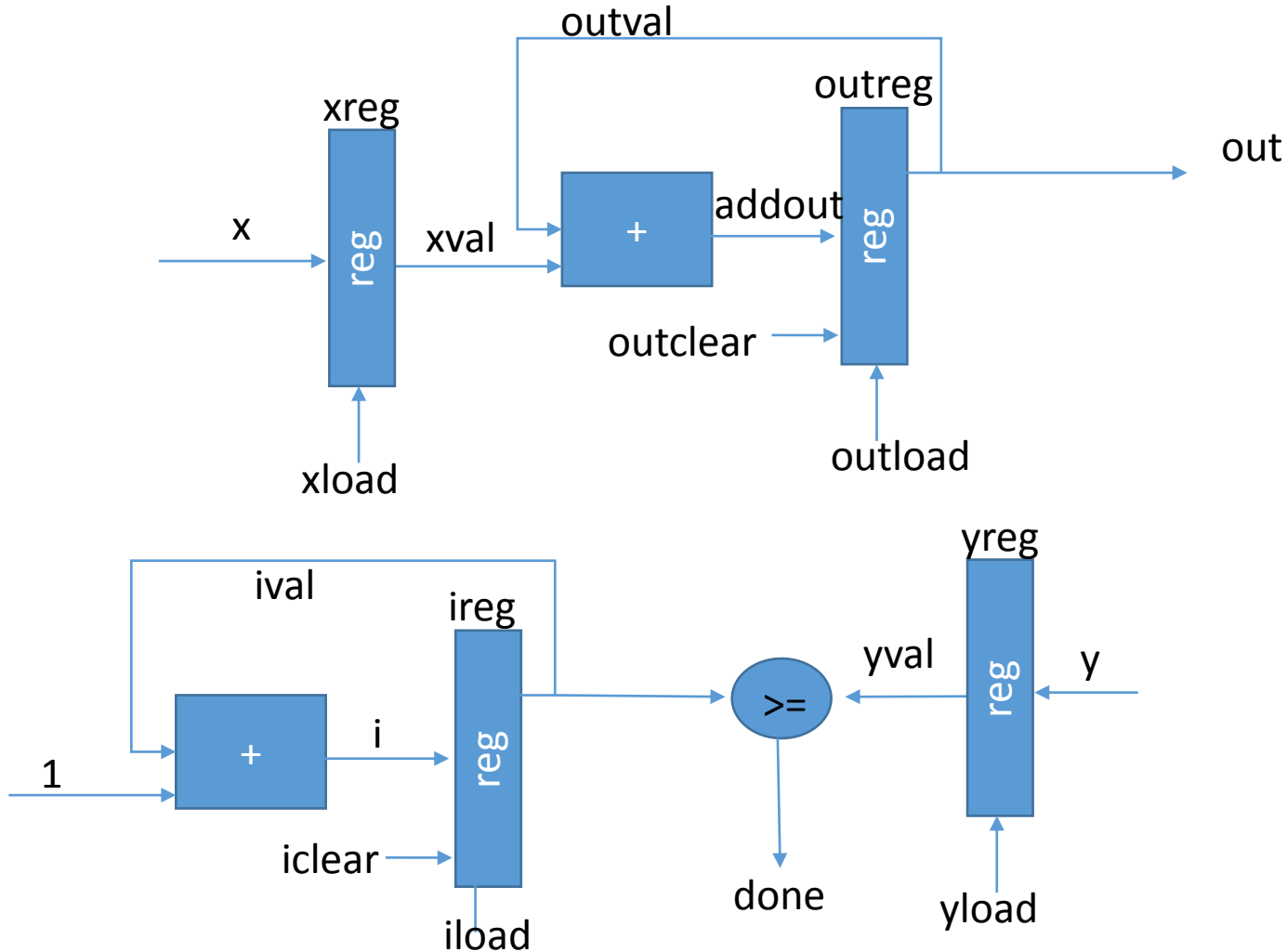Better Solution: Use One Adder Repeatedly




```
module increment
# (parameter W = 8)
(input [W-1:0] in1,
output reg [W-1:0] out);
```

```
always @ (*) begin
    out = in1 + 1;
end
endmodule
```


```
module comparator
# (parameter W = 8)
(input [W-1:0] ival,
input [W-1:0] yval,
output reg done);
```

```
always @ (*) begin
    done = 0;
    if (ival >= yval ) //Yes?
        done=1;
end
endmodule
```

How to Control the Datapath?

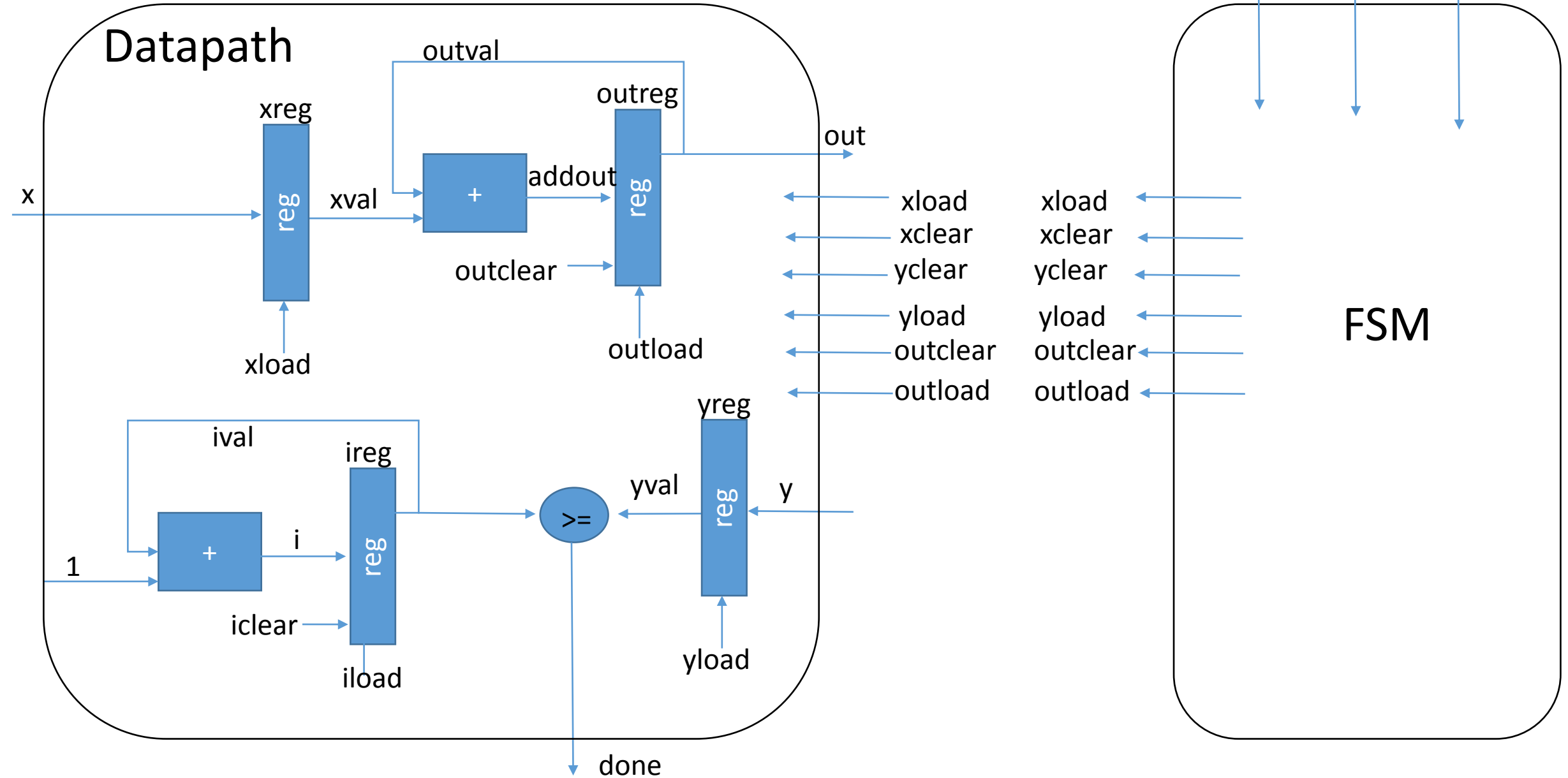

FSM States

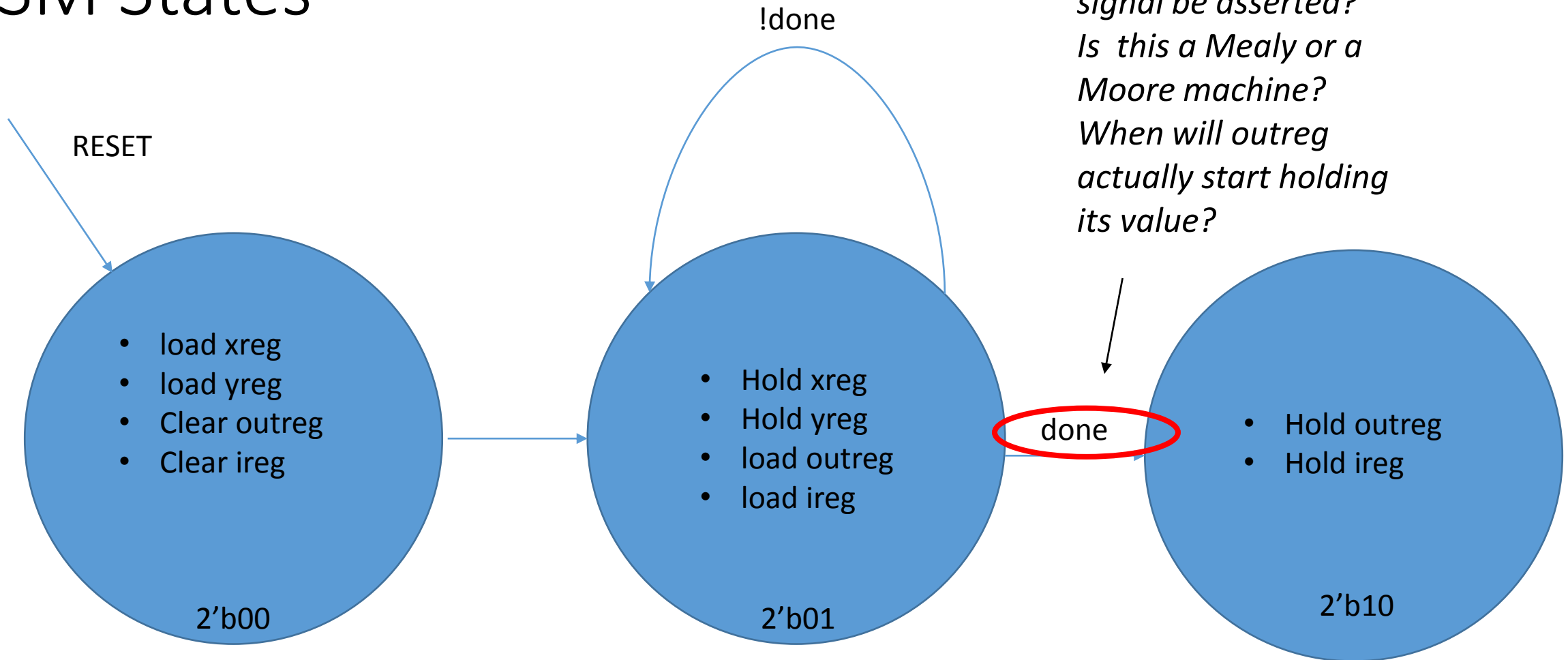

Increment Module

```
module comparator
# (parameter W = 8)
(input [W-1:0] ival,
 input [W-1:0] yval,
 output reg done);

always @ (*) begin
    done = 0;
    if (ival +1  >= yval -1 )
        done=1;
end
endmodule
```

Note:

- ival starts from 0 instead of 1
- When done signal is asserted, outreg only stops loading in the next clock cycle

Putting it All Together

```
module multiplier
# (parameter W = 8)
(input [W-1:0] x, input [W-1:0] y, input clk, input reset, output [2*W-1:0] out);

//variable declarations. Question: what datatype for xval, xclear, xload?

assign out = addout;

myreg #(W) xreg(x, xload, xclear, clk, xval); //xreg
myreg #(W) yreg(y, yload, yclear, clk, yval); //yreg
myreg #(2*W) outreg(addout, outload, outclear, clk, outval); //outreg
myreg #(W) ireg(i, iload, iclear, clk, ival); //ireg

adder #(W) add1 (xval, outval, addout); //out = out+x
increment incl (ival, i); //i = i+1
comparator #(W) comp1 (ival, yval, done); //i+1 >= y-1

myfsm fsm1 ( clk, reset, done, xload, xclear, yload, yclear, iload, iclear,
outload, outclear); //controller

endmodule
```

FSM Design (In-Class Exercise)

```
module myfsm (input clk, input reset, input done, output reg xload, output...);

reg [2:0] cs, ns;

always @ (posedge clk, posedge reset) begin
    //SEQUENTIAL PORTION: YOUR CODE HERE
end


always @(*) begin
    ns = cs;
    xload = 0; yload = 0;  iload =  0;  outload = 0;
    xclear = 0; yclear = 0; iclear = 0; outclear = 0;
    case (cs)
        2'b00 : begin
            // YOUR CODE HERE
        end
        2'b01: begin
            //YOUR CODE HERE
        end
        2'b10 : begin
            // YOUR CODE HERE
        end
        default :
    endcase
end
endmodule
```

Solution

```
case (cs)
    //START
    2'b00 : begin
        xload = 1; yload = 1;  iclear = 1; outclear = 1;
        ns = 2'b01;
    end
    //working
    2'b01: begin
        xload = 0; yload = 0;  iload = 1; outload = 1;
        if (done)
            ns = 2'b10;
        end
    //finished
    2'b10 : begin
        iload = 0; outload = 0;
    end

    default :  // put in don't cares
```

Desired Simulation Output

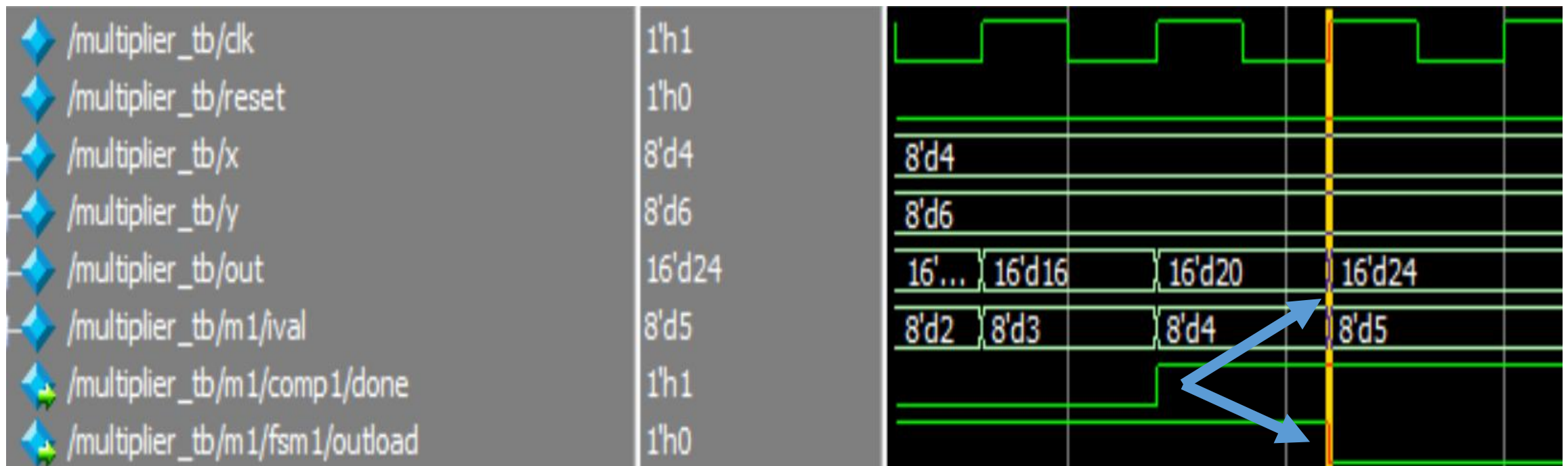

One clock cycle difference. Think of done as “almost done”